

5)


$$a) \quad \left. \begin{array}{l} V_1 = 1 \\ V_5 = 0 \end{array} \right\} \text{imposed}$$

$$\frac{(V_{i-1} - V_i)}{R} + \frac{(V_{i+1} - V_i)}{R} = 0 \quad \text{for } i=2,3,4 \quad (\text{no net current})$$

$$V_{i-1} - 2V_i + V_{i+1} = 0$$

$$\begin{pmatrix} 1 & 0 & 0 & 0 & 0 \\ 1 & -2 & 1 & 0 & 0 \\ 0 & 1 & -2 & 1 & 0 \\ 0 & 0 & 1 & -2 & 1 \\ 0 & 0 & 0 & 0 & 1 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{pmatrix} = \begin{pmatrix} 1 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix}$$

6) a)

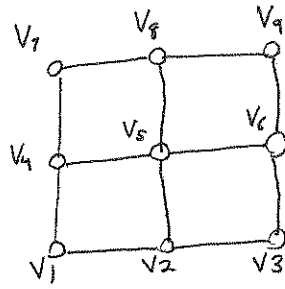

$$\left. \begin{array}{l} V_1 = 1 \\ V_9 = 0 \end{array} \right\} \text{imposed}$$

$$\text{For } i = 2 \dots 8 \quad \left. \sum_{j \text{ a neighbor of } i} \frac{(V_j - V_i)}{R} = 0 \right\} \text{net current into any node is } 0$$

$$i = 2 \quad (V_1 - V_2) + (V_5 - V_2) + (V_3 - V_2) = 0$$

$$i = 3 \quad (V_2 - V_3) + (V_6 - V_3) = 0$$

$$i = 4 \quad (V_1 - V_4) + (V_5 - V_4) + (V_7 - V_4) = 0$$

$$i = 5 \quad (V_2 - V_5) + (V_4 - V_5) + (V_6 - V_5) + (V_8 - V_5) = 0$$

$$i = 6 \quad (V_5 - V_6) + (V_9 - V_6) = 0$$

$$i = 7 \quad (V_4 - V_7) + (V_8 - V_7) = 0$$

$$i = 8 \quad (V_5 - V_8) + (V_7 - V_8) + (V_9 - V_8) = 0$$

In matrix form:

$$\begin{pmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 1 & -3 & 1 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & -2 & 0 & 0 & 1 & 0 & 0 & 0 \\ 1 & 0 & 0 & -3 & 1 & 0 & 1 & 0 & 0 \\ 0 & 1 & 0 & 1 & -4 & 1 & 0 & 1 & 0 \\ 0 & 0 & 1 & 0 & 1 & -3 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 & 0 & 0 & -2 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 1 & -3 & 1 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ V_6 \\ V_7 \\ V_8 \\ V_9 \end{pmatrix} = \begin{pmatrix} 1 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix}$$